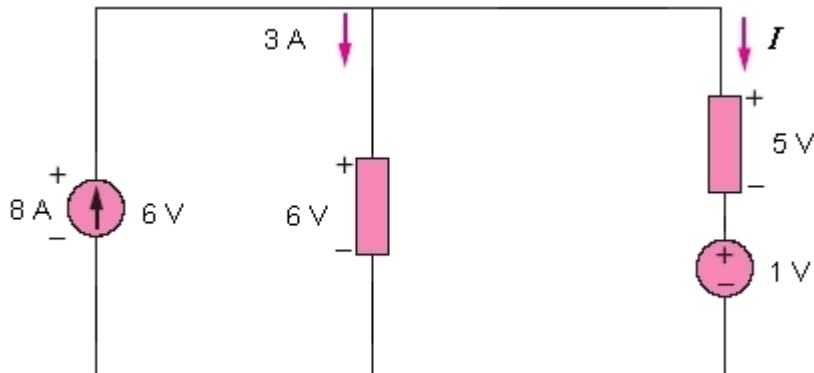


Question 1

Find I in the network shown below. (Round your answer to 2 decimal digits if necessary.)



$I = \underline{\hspace{1cm}} \text{ A}$


Question 2

A 2.3-kW toaster takes roughly 5 minutes to heat four slices of bread. Find the cost of operating the toaster once per day for 1 month (30 days). Assume energy costs 10 cents/kWh. (Round your answer to 2 decimal digits if necessary.)

Cost = $\underline{\hspace{1cm}}$ cents

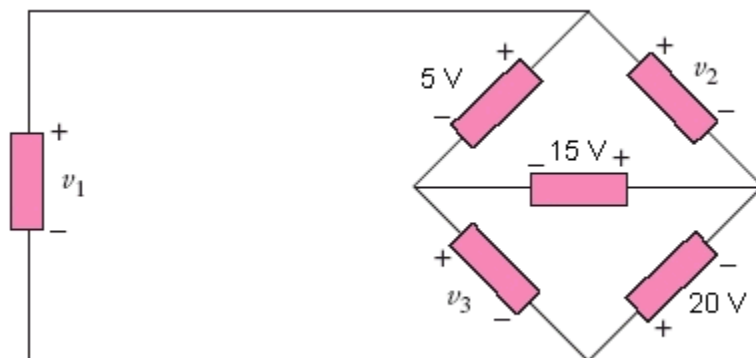Question 3

Find v_1 , v_2 , and v_3 in the circuit shown below.




$v_1 = \underline{\hspace{1cm}} \text{ V}$

$v_2 = \underline{\hspace{1cm}} \text{ V}$

$v_3 = \underline{\hspace{1cm}} \text{ V}$

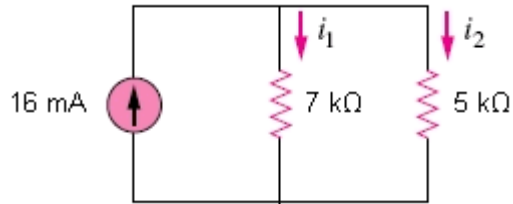Question 4

For the circuit shown below find i_1 and i_2 .
Round to two decimal places if necessary.




$$i_1 = \text{ ____ } \text{ mA}$$

$$i_2 = \text{ ____ } \text{ mA}$$

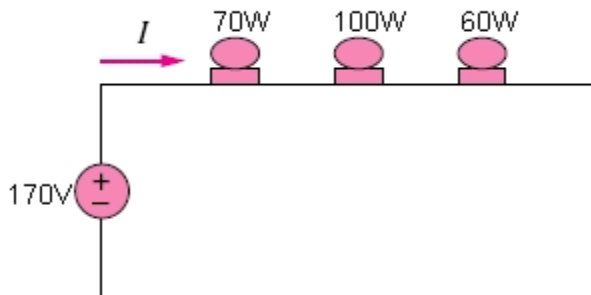Question 5


Three lightbulbs are connected in series to a 170-V battery as shown in the figure below. Find the current I through the bulbs. (Round your answer to 2 decimal digits if necessary.)



$$i = \text{ ____ } \text{ A}$$

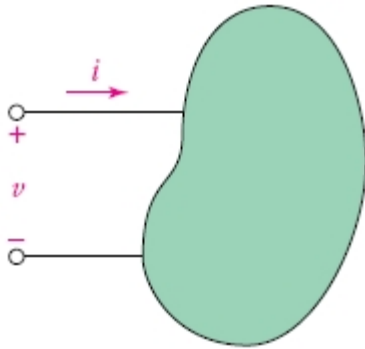Question 6


Let $i = 8te^{-150t}$ mA and $v = (0.006 - 0.2t)e^{-150t}$ V for the circuit element shown below. How much energy is delivered to the element in the interval $0 < t < \infty$? Round to two decimal places.



Energy = ____ $\times 10^{-7}$ mJ

Question 7

In the circuit shown below

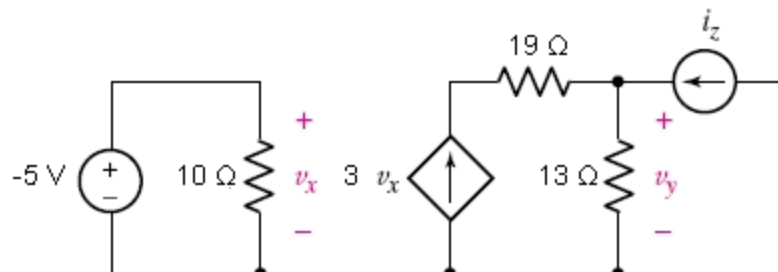


Calculate v_y if $i_z = 14$ A. (Round to 2 decimal places.)

$v_y =$ ____ V

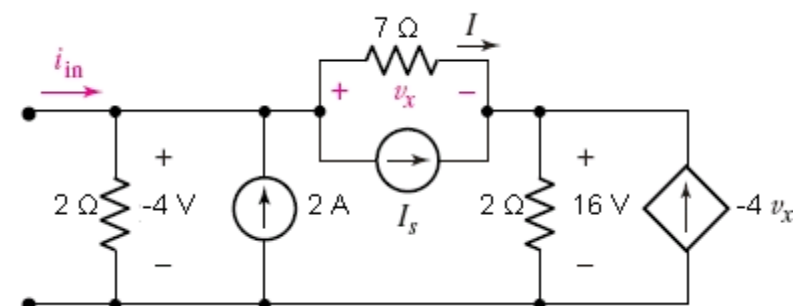Question 8


Use Ohm's and Kirchoff's laws on the circuit shown below to find i_{in} . (Round your final answer to a whole number if necessary.)



$i_{in} =$ ____ A


Question 9

Using combinations of sources, compute i for the circuit in the figure below.

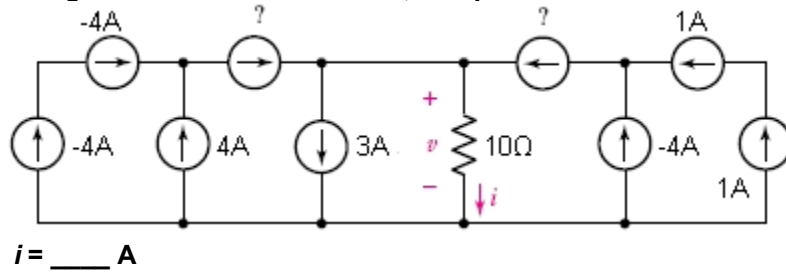


Question 10

In the circuit shown below, choose v_1 to obtain a current i_x of -3 A

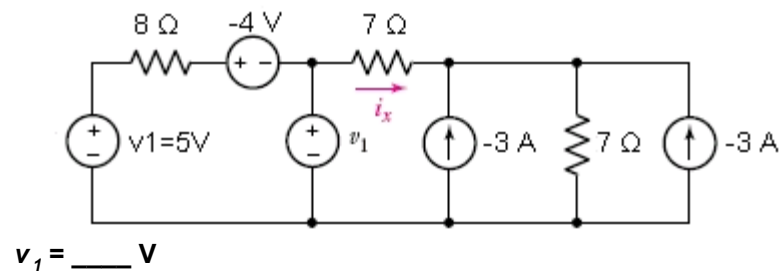

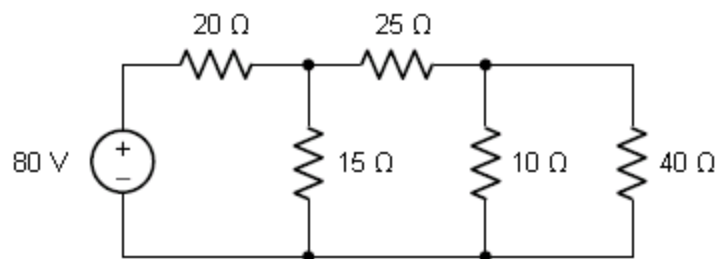Question 11

Find the power absorbed by each of the resistors in the circuit shown below. Round all calculations to two decimal places.



$$P_{20\Omega} = \underline{\hspace{1cm}} \text{ W}$$

$$P_{15\Omega} = \underline{\hspace{1cm}} \text{ W}$$

$$P_{25\Omega} = \underline{\hspace{1cm}} \text{ W}$$

$$P_{10\Omega} = \underline{\hspace{1cm}} \text{ W}$$

$$P_{40\Omega} = \underline{\hspace{1cm}} \text{ W}$$